 


على عطا الله

CA2

810199461




b) not # (7,9) not if # (14,18,16)

to 1 abst:

to 0: 1001 → 1011 to 2: 1111 → 1110

0101 → 0111

 

c) to 1

d) delay in systemverilog is 38 and in 0111 → 0101 transition

```
`timescale 1ns/1ns
module not_ (input c,output w2);
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T5(w2,Vdd,c);
    nmos #(3,5,7) T6(w2,Gnd,c);
endmodule

module not_ctrl_ (input c,EN1,output w1);
    wire i1,i2,i3;
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T1(i2,Vdd,c);
    pmos #(4,7,9) T2(w1,i2,i1);
    pmos #(4,7,9) T3(i1,Vdd,EN1);
    nmos #(3,5,7) T4(i1,Gnd,EN1);
    nmos #(3,5,7) T5(w1,i3,EN1);
    nmos #(3,5,7) T6(i3,Gnd,c);
endmodule
```

```

module CA2_E1 (input a,b,s,t,output w);
    wire i,j;
    not_ not1(s,i);
    not_ctrl_ nif1(a,i,j);
    not_ctrl_ nif2(b,s,j);
    not_ctrl_ nif3(j,t,w);
endmodule


```

TESTBENCH:

```

`timescale 1ns/1ns
module CA2_E1_TB ();
    logic aa=0,bb=1,ss=0,tt=1;
    wire ww;
    CA2_E1 eee(aa,bb,ss,tt,ww);
    initial begin
        #1000 ss=1;
        #1000 ss=0;
        #500 bb=0;
        #500 tt=0;
        #1000 $stop;
    end
endmodule


```

 

b) 2-to-1 multiplexer # (39, 43, 16)

to 1 abcdst: 01100 → 01110

to 0 abcdst: 10100 → 10110

 

c)
d) like 1-cd

```

`timescale 1ns/1ns
module not_ (input c,output w2);
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T5(w2,Vdd,c);
    nmos #(3,5,7) T6(w2,Gnd,c);
endmodule

module not_ctrl_ (input c,EN1,output w1);
    wire i1,i2,i3;
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T1(i2,Vdd,c);
    pmos #(4,7,9) T2(w1,i2,i1);
    pmos #(4,7,9) T3(i1,Vdd,EN1);
    nmos #(3,5,7) T4(i1,Gnd,EN1);
    nmos #(3,5,7) T5(w1,i3,EN1);
    nmos #(3,5,7) T6(i3,Gnd,c);
endmodule

module CA2_E1 (input a,b,s,t,output w);
    wire i,j;
    not_ not1(s,i);
    not_ctrl_ nif1(a,i,j);
    not_ctrl_ nif2(b,s,j);
    not_ctrl_ nif3(j,t,w);
endmodule

module CA2_E2 (input a,b,c,d,s,t,output w);
    wire i;
    not_ not1(t,i);
    CA2_E1 multi1(a,b,s,i,w);
    CA2_E1 multi2(c,d,s,t,w);
endmodule


```

TESTBENCH:

```

`timescale 1ns/1ns
module CA2_E2_TB ();
    logic aa=0,bb=1,cc=1,dd=1,ss=0,tt=0;
    wire ww;
    CA2_E2 eee(aa,bb,cc,dd,ss,tt,ww);
    initial begin
        #1000 ss=1;
        #1000 ss=0;
        #1000 $stop;
    end
endmodule


```

 

b) because 2-to-1 multiplexers are not series and their delays are independent to each other and worst case ^{delays} ~~case~~ of 8 multiplexers belongs to 1 multiplexers. the

c)

d) like 1-d, 2-d differences:

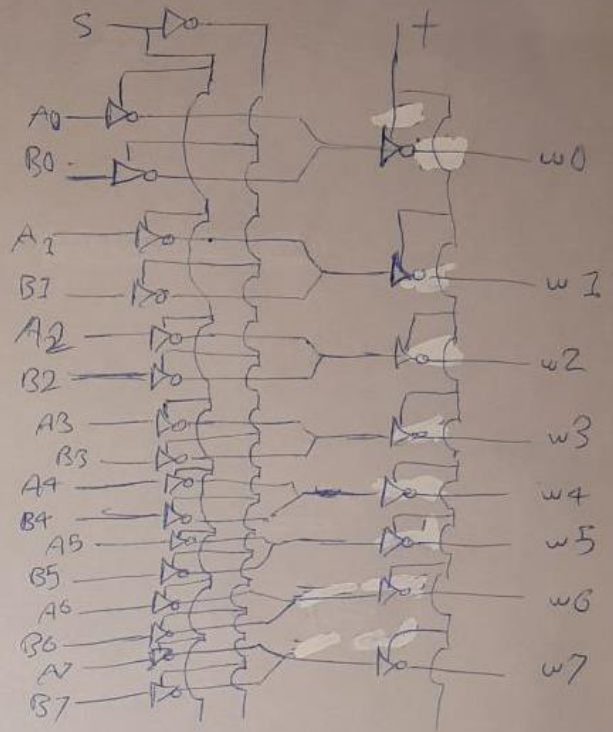

```

`timescale 1ns/1ns
module not_ (input c,output w2);
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T5(w2,Vdd,c);
    nmos #(3,5,7) T6(w2,Gnd,c);
endmodule

module not_ctrl_ (input c,EN1,output w1);
    wire i1,i2,i3;
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T1(i2,Vdd,c);
    pmos #(4,7,9) T2(w1,i2,i1);
    pmos #(4,7,9) T3(i1,Vdd,EN1);
    nmos #(3,5,7) T4(i1,Gnd,EN1);
    nmos #(3,5,7) T5(w1,i3,EN1);
    nmos #(3,5,7) T6(i3,Gnd,c);
endmodule

module CA2_E1 (input a,b,s,t,output w);
    wire i,j;
    not_ not1(s,i);
    not_ctrl_ nif1(a,i,j);
    not_ctrl_ nif2(b,s,j);
    not_ctrl_ nif3(j,t,w);
endmodule

```

```

module CA2_E3 (input [0:7]a,[0:7]b,input s,t,output [0:7]w);
    CA2_E1 e0(a[0],b[0],s,t,w[0]);
    CA2_E1 e1(a[1],b[1],s,t,w[1]);
    CA2_E1 e2(a[2],b[2],s,t,w[2]);
    CA2_E1 e3(a[3],b[3],s,t,w[3]);
    CA2_E1 e4(a[4],b[4],s,t,w[4]);
    CA2_E1 e5(a[5],b[5],s,t,w[5]);
    CA2_E1 e6(a[6],b[6],s,t,w[6]);
    CA2_E1 e7(a[7],b[7],s,t,w[7]);
endmodule

module CA2_E3_2 (input [0:7]a,[0:7]b,input s,t,output [0:7]w);
    assign w= ~s ? a : b ;
endmodule



```

testbench:

```

`timescale 1ns/1ns
module CA2_E3_TB ();
    logic [0:7] aa,bb;
    logic tt=1,ss=0;
    assign aa=8'b01110001;
    assign bb=8'b10100111;
    wire [0:7] ww;
    wire [7:0] wwassign;
    CA2_E3 eee(aa,bb,ss,tt,ww);
    CA2_E3_2 eeee(aa,bb,ss,tt,wwassign);
    initial begin
        #1000 ss=1;
        #1000 ss=0;
        #1000 $stop;
    end
endmodule

```

  880199461


worst case delay for a slice:

AB: 00 \rightarrow 01

$$\text{delay} = \max(9 + 25, 9 + 8) = 34$$

in one slice we can change A
 
$$\text{so delay} = \max(18, 25) = 25 \text{ ns}$$



c)

verify: the testbench shows that max delay of 1 slice is 34 ns

d) the max delay we calculate by hand is 8×34 but in testbench is 200 ns

```

`timescale 1ns/1ns
module slice (input a,b,output w2,w1);
    wire i;
    not #(7,9) not1(i,b);
    xor #(15,25) xor1(w2,a,i);
    nor #(8,18) nor1(w1,a,i);
endmodule

module complimentor8_bit (input [7:0] a,output [7:0] w);
    supply1 Vdd;
    wire i[7:0];
    slice slice0(a[0],Vdd,w[0],i[0]);
    slice slice1(a[1],i[0],w[1],i[1]);
    slice slice2(a[2],i[1],w[2],i[2]);
    slice slice3(a[3],i[2],w[3],i[3]);
    slice slice4(a[4],i[3],w[4],i[4]);
    slice slice5(a[5],i[4],w[5],i[5]);
    slice slice6(a[6],i[5],w[6],i[6]);
    slice slice7(a[7],i[6],w[7],i[7]);
endmodule

```

testbench:


```

`timescale 1ns/1ns
module CA2_E4_TB ();
    logic [0:7] aa;
    assign aa=8'b10000010;
    wire [7:0] ww1,ww2;
    complimentor8_bit eee(aa,ww1);
    assign #(34*8) ww2 = ~aa + 1'b1;
    initial begin
        #1000 $stop;
    end
endmodule

module CA2_E4_TB_1slice ();
    logic aa=0,bb=0;
    wire ww1,ww2;
    slice eee(aa,bb,ww2,ww1);
    initial begin
        #1000 bb=1;
        #500 bb=0;
        #500 aa=1;
        #1000 $stop;
    end
endmodule

```

5 - a)

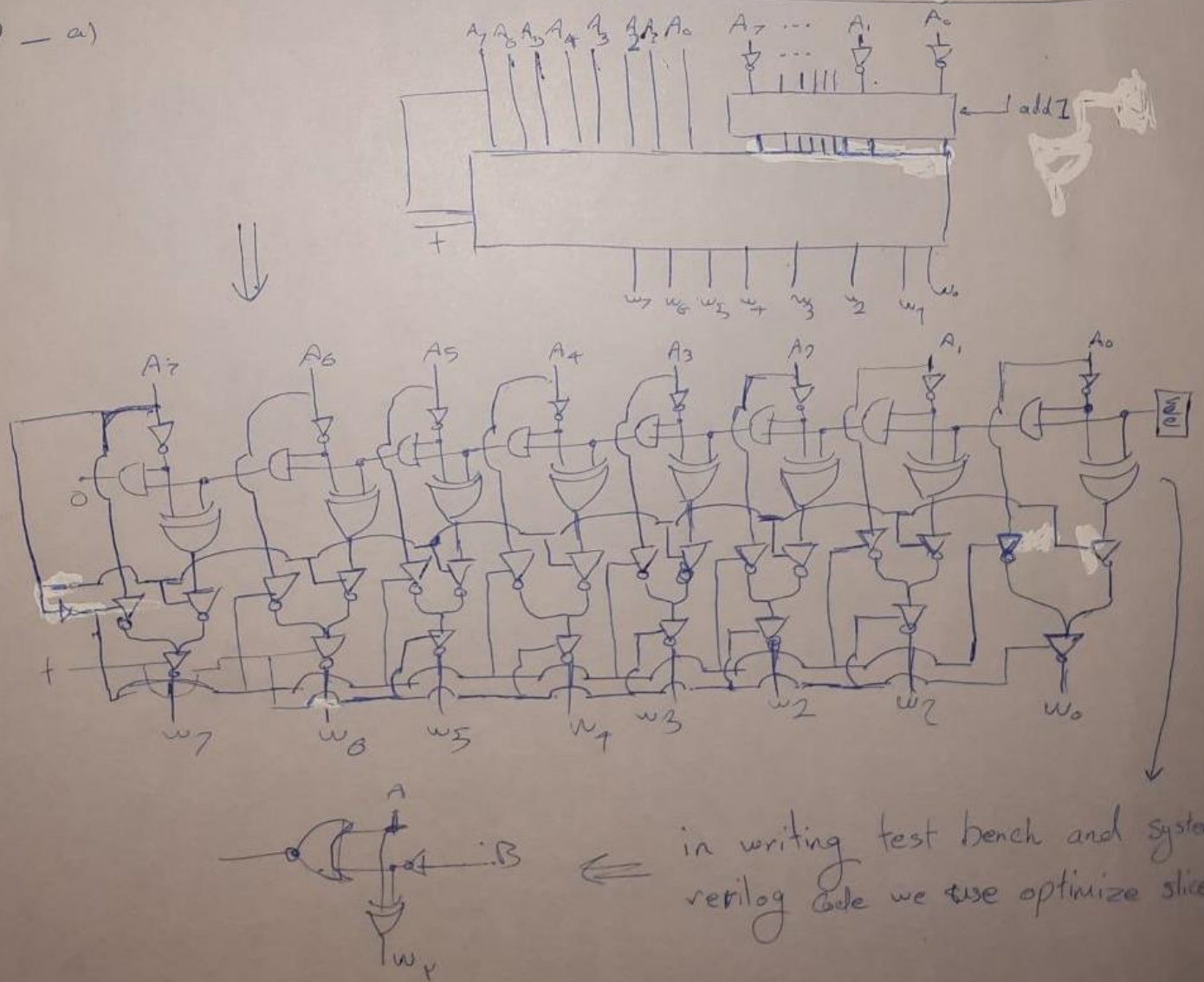

in writing test bench and system verilog code we use optimize slice

b) 2-to-2 multiplexer # (39, 43, 16)

worst delay of two's complementor section is 200

and it occurred when 10000001 entered so we enter 10000001

$$\rightarrow 200 + 14 + 18 = 232 \text{ ns}$$

تفاوت تعداد گیت یوسیس و برای ما:

برای ما: $3*8+3*8=48$

یوسییس: $12+25+12+1=50$

تفاوت 2 تا

```
`timescale 1ns/1ns
module not_ (input c,output w2);
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T5(w2,Vdd,c);
    nmos #(3,5,7) T6(w2,Gnd,c);
endmodule
module not_ctrl_ (input c,EN1,output w1);
    wire i1,i2,i3;
    supply1 Vdd;
    supply0 Gnd;
    pmos #(4,7,9) T1(i2,Vdd,c);
    pmos #(4,7,9) T2(w1,i2,i1);
    pmos #(4,7,9) T3(i1,Vdd,EN1);
    nmos #(3,5,7) T4(i1,Gnd,EN1);
    nmos #(3,5,7) T5(w1,i3,EN1);
    nmos #(3,5,7) T6(i3,Gnd,c);
endmodule
module CA2_E1 (input a,b,s,t,output w);
    wire i,j;
    not_ not1(s,i);
    not_ctrl_ nif1(a,i,j);
    not_ctrl_ nif2(b,s,j);
    not_ctrl_ nif3(j,t,w);
endmodule
module CA2_E3 (input [7:0]a,[7:0]b,s,t,output [7:0]w);
    CA2_E1 e0(a[0],b[0],s,t,w[0]);
    CA2_E1 e1(a[1],b[1],s,t,w[1]);
    CA2_E1 e2(a[2],b[2],s,t,w[2]);
    CA2_E1 e3(a[3],b[3],s,t,w[3]);
    CA2_E1 e4(a[4],b[4],s,t,w[4]);
    CA2_E1 e5(a[5],b[5],s,t,w[5]);
    CA2_E1 e6(a[6],b[6],s,t,w[6]);
    CA2_E1 e7(a[7],b[7],s,t,w[7]);
endmodule
module slice (input a,b,output w2,w1);
    wire i;
    not #(7,9) not1(i,b);
    xor #(15,25) xor1(w2,a,i);
    nor #(8,18) nor1(w1,a,i);
endmodule
```

```

module complimentor8_bit (input [7:0] a,output [7:0] w);
    supply1 Vdd;
    wire i[7:0];
    slice slice0(a[0],Vdd,w[0],i[0]);
    slice slice1(a[1],i[0],w[1],i[1]);
    slice slice2(a[2],i[1],w[2],i[2]);
    slice slice3(a[3],i[2],w[3],i[3]);
    slice slice4(a[4],i[3],w[4],i[4]);
    slice slice5(a[5],i[4],w[5],i[5]);
    slice slice6(a[6],i[5],w[6],i[6]);
    slice slice7(a[7],i[6],w[7],i[7]);
endmodule

module abs (input [7:0] aa,output [7:0] ww);
    wire [7:0] ii;
    supply1 Vdd;
    complimentor8_bit ee(aa,ii);
    CA2_E3 eee(aa,ii,aa[7],Vdd,ww);
endmodule

module abs_assign (input [7:0] aa,output [7:0] ww);
    assign #(8*25+32) ww = aa[7] ? ~aa + 1'b1 : aa;
endmodule

```

testbench:

```

`timescale 1ns/1ns
module CA2_E5_TB ();
    logic [7:0] aa;
    assign aa=8'b10000001;
    wire [7:0] ww1,ww2;
    abs eee(aa,ww1);
    abs_assign eeee(aa,ww2);
    initial begin
        #1000 $stop;
    end
endmodule

```

Yosys:

```

/* Generated by Yosys 0.7 (git sha1 61f6811, i686-w64-mingw32.static-gcc 4.9.3 -Os) */

module abs_assign(aa, ww);
    wire _000_;
    wire _001_;
    wire _002_;
    wire _003_;

```

```
wire _004_;
wire _005_;
wire _006_;
wire _007_;
wire _008_;
wire _009_;
wire _010_;
wire _011_;
wire _012_;
wire _013_;
wire _014_;
wire _015_;
wire _016_;
wire _017_;
wire _018_;
wire _019_;
wire _020_;
wire _021_;
wire _022_;
wire _023_;
wire _024_;
wire _025_;
wire _026_;
wire _027_;
wire _028_;
wire _029_;
wire _030_;
wire _031_;
wire _032_;
wire _033_;
wire _034_;
wire _035_;
wire _036_;
wire _037_;
wire _038_;
wire _039_;
wire _040_;
wire _041_;
wire _042_;
wire _043_;
wire _044_;
wire _045_;
wire _046_;
wire _047_;
wire _048_;
wire _049_;
wire _050_;
wire _051_;
wire _052_;
wire _053_;
```

```
wire _054_;
wire _055_;
wire _056_;
wire _057_;
wire _058_;
wire _059_;
wire _060_;
wire _061_;
wire _062_;
wire _063_;
wire _064_;
wire _065_;
wire _066_;
wire _067_;
wire _068_;
wire _069_;
wire _070_;
wire _071_;
wire _072_;
wire _073_;
wire _074_;
wire _075_;
input [7:0] aa;
output [7:0] ww;
NOT _076_ (
    .A(_018_),
    .Y(_023_)
);
NAND _077_ (
    .A(_070_),
    .B(_023_),
    .Y(_024_)
);
NAND _078_ (
    .A(_070_),
    .B(_027_),
    .Y(_026_)
);
NOR _079_ (
    .A(_070_),
    .B(_027_),
    .Y(_028_)
);
NOR _080_ (
    .A(_028_),
    .B(_023_),
    .Y(_030_)
);
NAND _081_ (
    .A(_030_),
```



```
.B(_026_),
.Y(_031_)
);
NAND _082_ (
.A(_031_),
.B(_024_),
.Y(_075_)
);
NOR _083_ (
.A(_030_),
.B(_019_),
.Y(_033_)
);
NOT _084_ (
.A(_019_),
.Y(_035_)
);
NOT _085_ (
.A(_030_),
.Y(_036_)
);
NOR _086_ (
.A(_036_),
.B(_035_),
.Y(_037_)
);
NOR _087_ (
.A(_037_),
.B(_033_),
.Y(_020_)
);
NOT _088_ (
.A(_021_),
.Y(_039_)
);
NOT _089_ (
.A(_027_),
.Y(_041_)
);
NOT _090_ (
.A(_070_),
.Y(_042_)
);
NAND _091_ (
.A(_042_),
.B(_041_),
.Y(_043_)
);
NOR _092_ (
.A(_043_),
```

```
.B(_019_),
.Y(_045_)
);
NOR _093_ (
.A(_045_),
.B(_023_),
.Y(_046_)
);
NOT _094_ (
.A(_046_),
.Y(_047_)
);
NOR _095_ (
.A(_047_),
.B(_039_),
.Y(_048_)
);
NOR _096_ (
.A(_046_),
.B(_021_),
.Y(_049_)
);
NOR _097_ (
.A(_049_),
.B(_048_),
.Y(_022_)
);
NOT _098_ (
.A(_025_),
.Y(_050_)
);
NAND _099_ (
.A(_028_),
.B(_035_),
.Y(_051_)
);
NOR _100_ (
.A(_051_),
.B(_021_),
.Y(_052_)
);
NOR _101_ (
.A(_052_),
.B(_023_),
.Y(_053_)
);
NOT _102_ (
.A(_053_),
.Y(_054_)
);
```

```
NOR _103_ (  
    .A(_054_),  
    .B(_050_),  
    .Y(_055_)  
);  
NOR _104_ (  
    .A(_053_),  
    .B(_025_),  
    .Y(_056_)  
);  
NOR _105_ (  
    .A(_056_),  
    .B(_055_),  
    .Y(_029_)  
);  
NOT _106_ (  
    .A(_032_),  
    .Y(_057_)  
);  
NAND _107_ (  
    .A(_052_),  
    .B(_050_),  
    .Y(_058_)  
);  
NAND _108_ (  
    .A(_058_),  
    .B(_018_),  
    .Y(_059_)  
);  
NOR _109_ (  
    .A(_059_),  
    .B(_057_),  
    .Y(_061_)  
);  
NOT _110_ (  
    .A(_059_),  
    .Y(_062_)  
);  
NOR _111_ (  
    .A(_062_),  
    .B(_032_),  
    .Y(_063_)  
);  
NOR _112_ (  
    .A(_063_),  
    .B(_061_),  
    .Y(_034_)  
);  
NOT _113_ (  
    .A(_038_),
```

```
.Y(_064_)
);
NAND _114_ (
    .A(_045_),
    .B(_039_),
    .Y(_065_)
);
NOR _115_ (
    .A(_065_),
    .B(_025_),
    .Y(_066_)
);
NAND _116_ (
    .A(_066_),
    .B(_057_),
    .Y(_067_)
);
NAND _117_ (
    .A(_067_),
    .B(_018_),
    .Y(_068_)
);
NOR _118_ (
    .A(_068_),
    .B(_064_),
    .Y(_069_)
);
NOR _119_ (
    .A(_058_),
    .B(_032_),
    .Y(_071_)
);
NOR _120_ (
    .A(_071_),
    .B(_023_),
    .Y(_072_)
);
NOR _121_ (
    .A(_072_),
    .B(_038_),
    .Y(_073_)
);
NOR _122_ (
    .A(_073_),
    .B(_069_),
    .Y(_040_)
);
NAND _123_ (
    .A(_064_),
    .B(_018_),
```



```
.Y(_074_)
);
NOR _124_ (
    .A(_074_),
    .B(_067_),
    .Y(_044_)
);
BUF _125_ (
    .A(_027_),
    .Y(_060_)
);
assign _018_ = aa[7];
assign _027_ = aa[0];
assign ww[0] = _060_;
assign _070_ = aa[1];
assign ww[1] = _075_;
assign _019_ = aa[2];
assign ww[2] = _020_;
assign _021_ = aa[3];
assign ww[3] = _022_;
assign _025_ = aa[4];
assign ww[4] = _029_;
assign _032_ = aa[5];
assign ww[5] = _034_;
assign _038_ = aa[6];
assign ww[6] = _040_;
assign ww[7] = _044_;
endmodule
```